

PHYS 1444 - Lecture 13
October 27, 2020
Luke Sweeney
UT Arlington

1 AC Circuits - Frequency Limits

We take the limit as the frequency gets high or low.

- High Frequency Limit (ω is very large): $\omega \rightarrow \infty$
-